



University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

VE 320 – Summer 2012 Introduction to Semiconductor Device

Introduction to Bipolar Transistors

Instructor: Professor Hua Bao

NANO ENERGY LAB

Bao Ve320 S12

1


Transistor

tran•sis•tor (trán-zis'ter)

A solid-state electronic device that is used to control the flow of electricity in electronic equipment and consists of a small block of a semiconductor with at least three electrodes

Trans(fer) + (res)istor

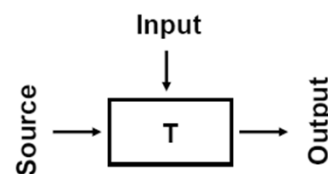Idea: control large output
with small input



This device should exhibit gain




University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

2

Background

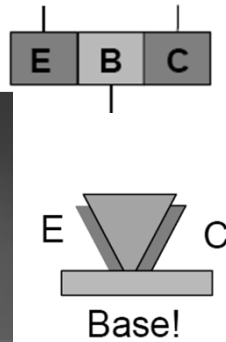

John Bardeen, William Shockley and Walter Brattain at Bell Labs, 1948.

Point contact Germanium transistor




University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

3

Shockley's Bipolar Transistors

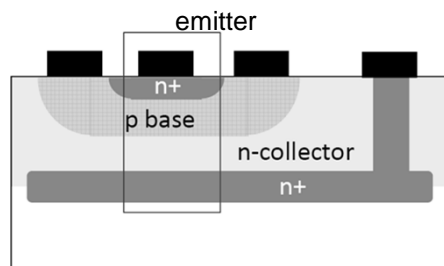

Double diffused BJT





University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

4

Terminals of BJT

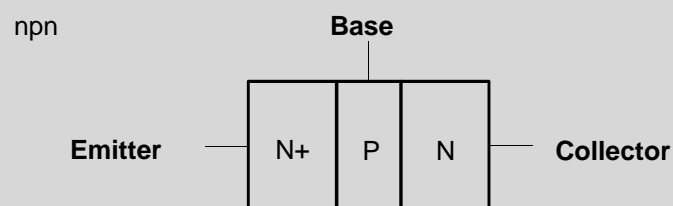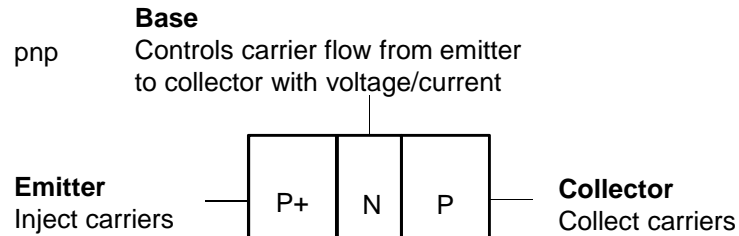


University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

5

Symbols and Convention

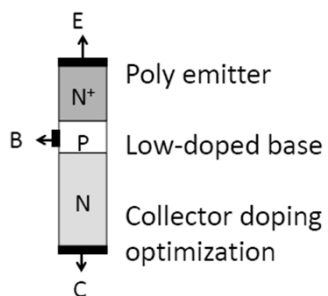


Depends on how you define...

$$I_E = I_B + I_C$$

$$V_{EB} + V_{BC} + V_{CE} = 0$$

Symbols

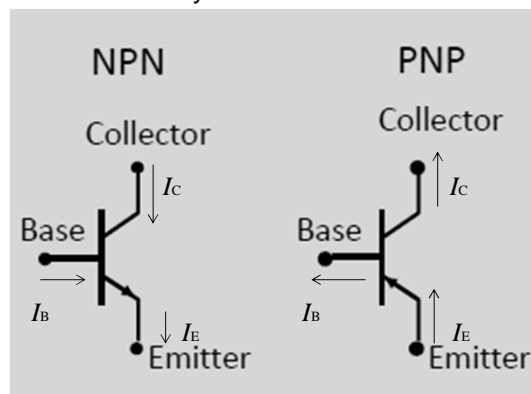


University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

6

Circuit Configuration (pnp)

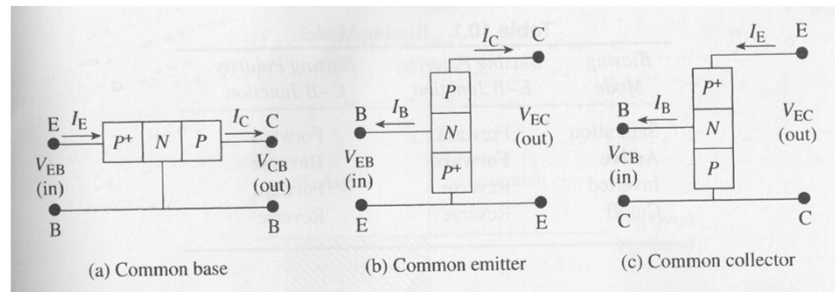

- Common emitter: most widely used
- Common collector: almost never used




University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12


7

Biasing Mode (pnp)

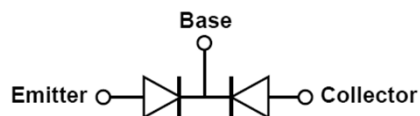- Two face to face p-n junctions
- Base voltage/current control hole current



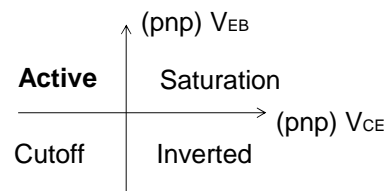Four regions of operation corresponding to forward/reverse bias of base-emitter and base-collector p-n junctions



Active: most widely encountered. Large signal gain and small signal distortion



University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

8

Electrostatics

$$\nabla \cdot \mathbf{D} = q(p - n + N_D^+ - N_A^-) \rightarrow \text{Electrostatic}$$

$$\frac{\partial n}{\partial t} = \frac{1}{q} \nabla \cdot \mathbf{J}_N - r_N + g_N$$

$$\mathbf{J}_N = qn\mu_N\mathcal{E} + qD_N\nabla n$$

$$\frac{\partial p}{\partial t} = -\frac{1}{q} \nabla \cdot \mathbf{J}_P - r_P + g_P$$

$$\mathbf{J}_P = qp\mu_P\mathcal{E} - qD_P\nabla p$$

DC/AC/Transient




University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

9

Band Diagram at Equilibrium (pnp)

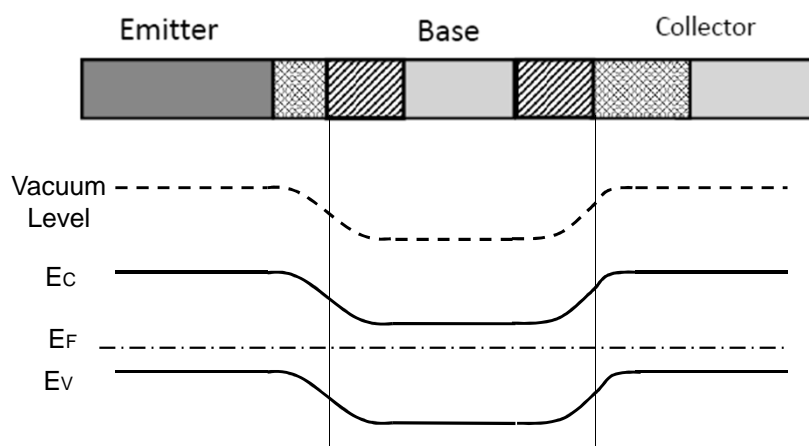


University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

10

Coordinates and Convention

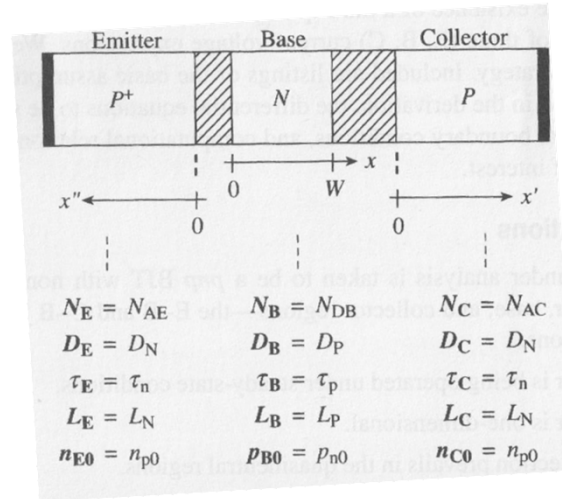

University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

11

Electrostatics in Equilibrium

$$x_{n,BE} = \sqrt{\frac{2K_S\epsilon_0}{q} \frac{N_E}{N_B(N_E + N_B)} V_{bi}}$$

$$x_{n,BC} = \sqrt{\frac{2K_S\epsilon_0}{q} \frac{N_C}{N_B(N_C + N_B)} V_{bi}}$$

$$x_{p,E} = \sqrt{\frac{2K_S\epsilon_0}{q} \frac{N_B}{N_E(N_B + N_E)} V_{bi}}$$

$$x_{p,C} = \sqrt{\frac{2K_S\epsilon_0}{q} \frac{N_B}{N_C(N_C + N_B)} V_{bi}}$$

The diagram shows the BJT structure with depletion widths $x_{n,BE}$, $x_{n,BC}$, $x_{p,E}$, and $x_{p,C}$ indicated. Below the structure, the potential and electric field profiles are shown, with the potential being continuous and the electric field having discontinuities at the junctions.




University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

12

Band Diagram with Bias (Active)

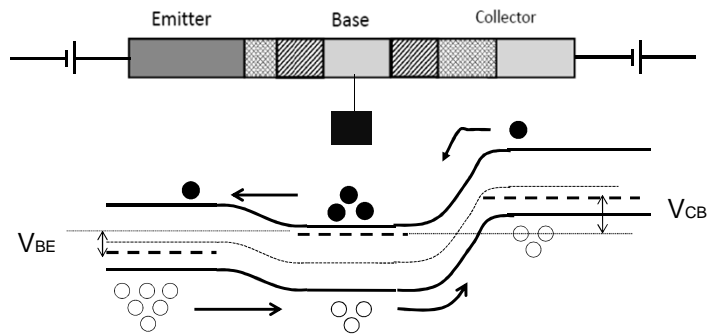

Depletion width of EB diode is reduced, CB diode is widened.

Equations are similar to the previous slides except that

$V_{bi} \rightarrow V_{bi} - V_{BE}$ at the E-B side

$V_{bi} \rightarrow V_{bi} - V_{BC}$ at C-B side




University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

13

Narrow Base

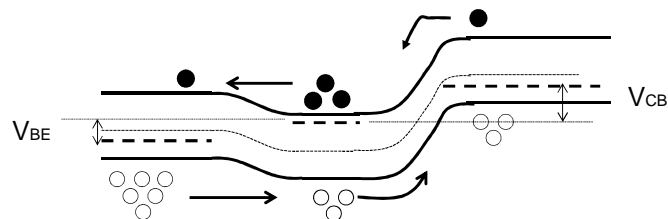

- Base is narrow comparing to minority carrier diffusion length
- Holes injected to the base almost completely diffused to the collector
- This is a BJT, not two back-to-back pn junctions




University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

14

More Details

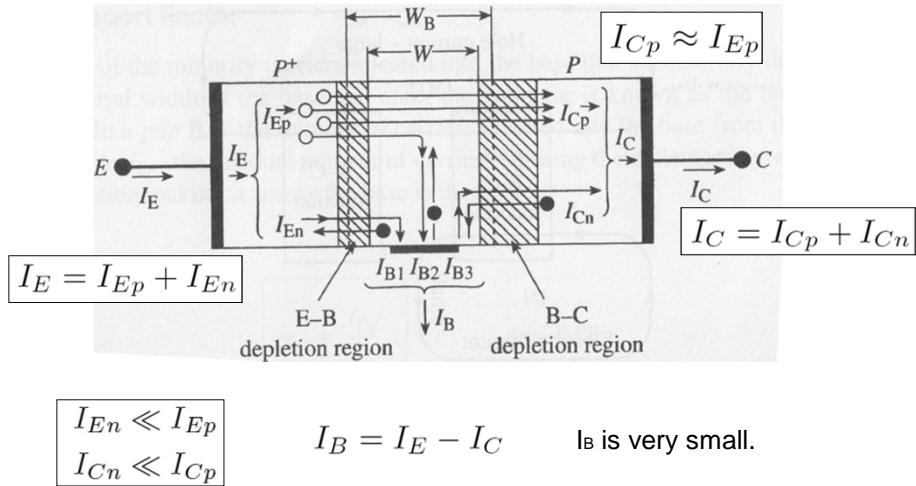


University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

15

Amplify a Signal

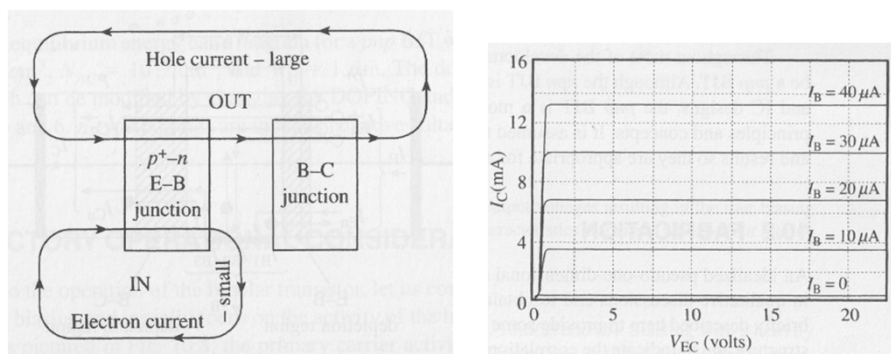

DC current gain is I_B/I_C



University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics


Bao Ve320 S12

16

Emitter Injection Efficiency

What fraction of the emitter current is due to the intended carrier injection?
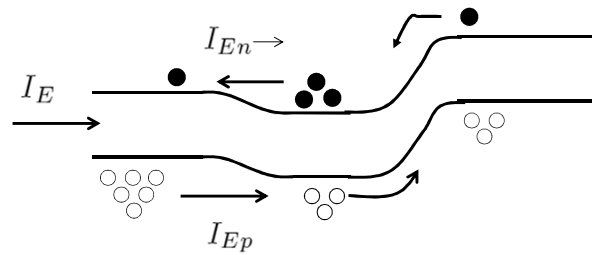
$$\gamma = \frac{I_{Ep}}{I_E} = \frac{I_{Ep}}{I_{Ep} + I_{En}}$$



Determined by doping levels and diffusion process.



University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics


Bao Ve320 S12

17

Base Transport Factor

What fraction of the injected electron shows up as collector current?

$$\alpha_T = \frac{I_{Cp}}{I_{Ep}}$$

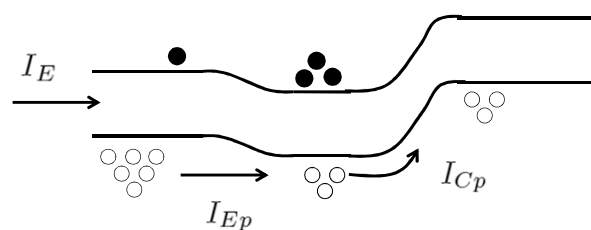

Determined by base width and carrier diffusion length in base



University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics


Bao Ve320 S12

18

Common Base d.c. Current Gain

How much of the emitter current shows up at the collector?
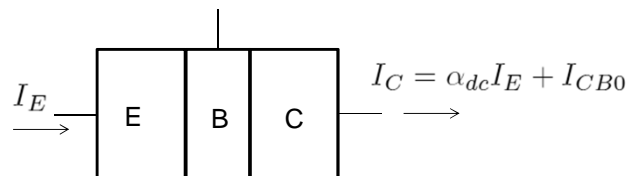
$$\alpha_{dc} = \gamma\alpha_T = \frac{I_{Cp}}{I_E} \approx \frac{I_C}{I_E}$$



Depends on emitter injection efficiency and base transport factor



University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics


Bao Ve320 S12

19

Common Emitter d.c. Current Gain

What is the output current (collector) relative to the input (base) current?
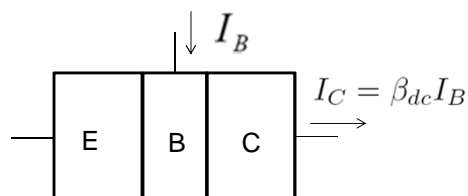
$$\beta = \frac{I_C}{I_B} = \frac{\alpha_{dc}}{1 - \alpha_{dc}}$$



Depends on emitter injection efficiency and base transport factor.



University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

20