

VE 320 – Summer 2012 Introduction to Semiconductor Device

Ideal BJT


Instructor: Professor Hua Bao

NANO ENERGY LAB

Bao Ve320 S12

1

Ideal BJT

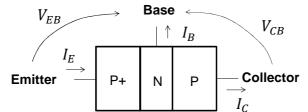


Assumptions:

- pnp device, step junction
- Steady state
- One dimensional
- · Low-level injection prevails in the quasineutral regions
- · No other process other than drift, diffusion, thermal R-G
- · Negligible thermal R-G in depleted regions
- Emitter and collector much larger than minority carrier diffusion length



Bao Ve320 S12

Coordinates and Convention

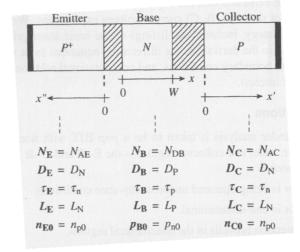


University of Michigan – Shanghai Jiao Tong University Joint Institute Center of Optics and Optoelectronics

Bao Ve320 S12

3

Equations and Boundary Conditions

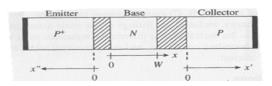

$$0 = D\frac{d^2 \Delta n}{dx^2} - \frac{\Delta n}{\tau} \qquad \Longrightarrow \qquad \Delta n(x) = C_1 e^{-x/L} + C_2 e^{x/L}$$

Boundary Conditions

Emitter: $\Delta n_E(x'' \to \infty) = 0$ $\Delta n_E(x'' = 0) = n_{E0}(e^{qV_{EB}/kT} - 1)$

Base: $\Delta p_B(0) = p_{B0}(e^{qV_{EB}/kT} - 1)$ $\Delta p_B(W) = p_{B0}(e^{qV_{CB}/kT} - 1)$

Collector: $\Delta n_C(x' \to \infty) = 0$ $\Delta n_C(x' = 0) = n_{C0}(e^{qV_{CB}/kT} - 1)$

University of Michigan – Shanghai Jiao Tong University Joint Institut

Center of Optics and Optoelectronics

Bao Ve320 S12


Solutions

It should not be surprising to see the solutions like the following...

$$\Delta n_E(x'') = n_{E0}(e^{qV_{EB}/kT} - 1)e^{-x''/L_E}$$

$$\Delta n_C(x') = n_{C0} (e^{qV_{CB}/kT} - 1)e^{-x'/L_C}$$
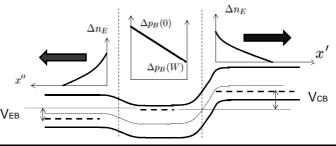
$$\Delta p_B(x) = \Delta p_B(0) \frac{\sinh[(W-x)/L_B]}{\sinh(W/L_B)} + \Delta p_B(W) \frac{\sinh(x/L_B)}{\sinh(W/L_B)}$$




University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

5

Currents

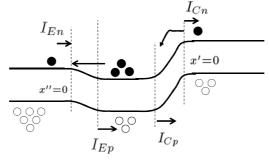


$$I_{En} = -qAD_E \frac{d\Delta n_E}{dx''} \mid_{x''=0} = qA \frac{D_E}{L_E} n_{E0} (e^{qV_{EB}/kT} - 1)$$

$$I_{Cn} = qAD_C \frac{d\Delta n_C}{dx'} \mid_{x'=0} = -qA \frac{D_C}{L_C} n_{C0} (e^{qV_{CB}/kT} - 1)$$

University of Michigan – Shanghai Jiao Tong University Joint Institut
Center of Optics and Optoelectronics

Bao Ve320 S12

Currents cont'd

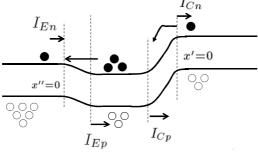

$$I_{Ep} = qA \frac{D_B}{L_B} p_{B0} \left[\frac{\cosh(W/L_B)}{\sinh(W/L_B)} (e^{qV_{EB}/kT} - 1) - \frac{1}{\sinh(W/L_B)} (e^{qV_{CB}/kT} - 1) \right]$$

$$I_{Cp} = qA \frac{D_B}{L_B} p_{B0} \left[\frac{1}{\sinh(W/L_B)} (e^{qV_{EB}/kT} - 1) - \frac{\cosh(W/L_B)}{\sinh(W/L_B)} (e^{qV_{CB}/kT} - 1) \right]$$

Under active mode biasing, VEB>0 and VCB<0, therefore the second term is very small comparing to the first term.



Bao Ve320 S12

7


Narrow Base

$$\Delta p_B(x) = \Delta p_B(0) \frac{\sinh[(W-x)/L_B]}{\sinh(W/L_B)} + \Delta p_B(W) \frac{\sinh(x/L_B)}{\sinh(W/L_B)}$$

Base width much smaller than minority carrier diffusion length.

$$W \ll L_B$$
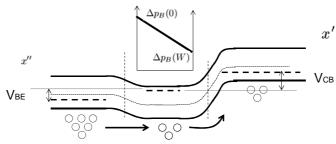
$$\Delta p_B(x) \approx \Delta p_B(0) \left(1 - \frac{x}{W}\right) + \Delta p_B(W) \frac{x}{W}$$



University of Michigan – Shanghai Jiao Tong University Joint Institut
Center of Optics and Optoelectronics

Bao Ve320 S12

Performance Parameters

$$\gamma = \frac{I_{Ep}}{I_E} = \frac{I_{Ep}}{I_{Ep} + I_{En}}$$

$$\alpha_T = \frac{I_{Cp}}{I_{Ep}}$$
 Solution of minority carrier diffusion equation
$$\alpha_{dc} = \gamma \alpha_T = \frac{I_{Cp}}{I_E} \approx \frac{I_C}{I_E}$$
 Narrow base

$$lpha_{dc} = \gamma lpha_T = rac{I_{Cp}}{I_E} pprox rac{I_C}{I_E}$$

$$\beta = \frac{I_C}{I_B} = \frac{\alpha_{dc}}{1 - \alpha_{dc}}$$

Solution of minority carrier diffusion equation

$$\begin{array}{c|c} \alpha & \alpha \\ \hline a \\ \hline \end{array}$$

$$\gamma = \frac{1}{1 + \frac{D_{E}}{D_{B}} \frac{N_{B}}{N_{E}} \frac{W}{L_{E}}}$$

$$\alpha_{T} = \frac{1}{1 + \frac{1}{2} \left(\frac{W}{L_{B}}\right)^{2}}$$

$$\alpha_{dc} = \frac{1}{1 + \frac{D_{E}}{D_{B}} \frac{N_{B}}{N_{E}} \frac{W}{L_{E}} + \frac{1}{2} \left(\frac{W}{L_{B}}\right)^{2}}$$

$$\beta_{dc} = \frac{1}{\frac{D_{E}}{D_{B}} \frac{N_{B}}{N_{E}} \frac{W}{L_{E}} + \frac{1}{2} \left(\frac{W}{L_{B}}\right)^{2}}$$

University of Michigan – Shanghai Jiao Tong University Joint Institute
Center of Optics and Optoelectronics

Bao Ve320 S12

9

Ebers-Moll Equations

$$I_{E} = qA \left[\left(\frac{D_{E}}{L_{E}} n_{E0} + \frac{D_{B}}{L_{B}} p_{B0} \frac{\cosh(W/L_{B})}{\sinh(W/L_{B})} \right) \left(e^{qV_{EB}/kT} - 1 \right) - \left(\frac{D_{B}}{L_{B}} p_{B0} \frac{1}{\sinh(W/L_{B})} \right) \left(e^{qV_{CB}/kT} - 1 \right) \right]$$

$$= \alpha_{R} I_{R0} \qquad \alpha_{F} I_{F0}$$

$$I_{C} = qA \left[\left(\frac{D_{B}}{L_{B}} p_{B0} \frac{1}{\sinh(W/L_{B})} \right) \left(e^{qV_{CB}/kT} - 1 \right) - \left(\frac{D_{C}}{L_{C}} n_{C0} + \frac{D_{B}}{L_{B}} p_{B0} \frac{\cosh(W/L_{B})}{\sinh(W/L_{B})} \right) \left(e^{qV_{CB}/kT} - 1 \right) \right]$$

$$= \alpha_{F} I_{F0} = \alpha_{R} I_{R0} = qA \frac{D_{B}}{L_{B}} \frac{p_{B0}}{\sinh(\frac{W}{L_{B}})}$$


$$\alpha_{F} I_{F0} = \alpha_{R} I_{R0} = qA \frac{D_{B}}{L_{B}} \frac{p_{B0}}{\sinh(\frac{W}{L_{B}})}$$

Center of Optics and Optoelectronics


Bao Ve320 S12

Ebers-Moll Equations

• Node equation for BJT terminals

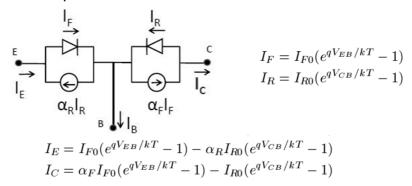

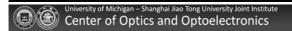The four parameters can be treated as empirical parameters.



Bao Ve320 S12